

C1, C3 = 0.013 uF, Mica
C2 = 0.023 uF, Mica
(Voltage rating of C1 ,2 ,3, depend on power level - 2 KV is suitable)
L1, L2 = 40 uHy
(22 turns #12 THHN wound on 4" OD thinwall PVC drain pipe)

NOTES:
--------

- -Filter Cut-Off frequency = 275 KC.
- -Filter is suitable for use between 70 KC 200 KC at power levels of up to 500 Watts CW.
- Mount coils at right angles to each other.
- Mount coils so that the sides of the coils are at
- least 1.5 2 inches away from metal panels.
- The filter is symmetrical, so either end may be used as input or output.
- The filter should be mounted in a shielded enclosure
- to prevent harmonic radiation. A steel cabinet is preferred.